

# Verilog HDL: Gate Level Modeling


**Pravin Zode**

# Outline

- Gate Level modeling
- Examples
 
# Gate Level Modeling

- Represents digital circuits using basic logic gate
- Works well for small circuits with a limited number of gates
- Intuitive for designers familiar with digital logic design
- Requires manual instantiation and connection of individual gates
- Common gate primitives: `and`, `or`, `nand`, `nor`, `xor`, `xnor`, `not`



# Truth Table for Gates

	<b>and</b>	i1			
		0	1	x	z
i2	0	0	0	0	0
	1	0	1	x	x
	x	0	x	x	x
	z	0	x	x	x

	<b>or</b>	i1			
		0	1	x	z
i2	0	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
	z	x	1	x	x


	<b>xor</b>	i1			
		0	1	x	z
i2	0	0	1	x	x
	1	1	0	x	x
	x	x	x	x	x
	z	x	x	x	x

	<b>nand</b>	i1			
		0	1	x	z
i2	0	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x


	<b>nor</b>	i1			
		0	1	x	z
i2	0	1	0	x	x
	1	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x

	<b>xnor</b>	i1			
		0	1	x	z
i2	0	1	0	x	x
	1	0	1	x	x
	x	x	x	x	x
	z	x	x	x	x

# Buffer and NOT Gate

 


buf	in	out
	0	0
	1	1
	x	x
	z	x

 


not	in	out
	0	1
	1	0
	x	x
	z	x

# Bufif Gate

 


		ctrl			
bufif1		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

 


		ctrl			
bufif0		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

```
bufif1 b1 (out, in, ctrl);
bufif0 b0 (out, in, ctrl);
```

# NOTif Gate

 

		ctrl			
notif1		0	1	x	z
in	0	z	1	H	H
	1	z	0	L	L
	x	z	x	x	x
	z	z	x	x	x

 

		ctrl			
notif0		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x



```
notif1 n1 (out, in, ctrl);
notif0 n0 (out, in, ctrl);
```

# Syntax

- Gates can have one or more inputs, one output


```
and g1(out, a, b);    // out = a AND b
```
  
```
not g2(y, x);         // y = NOT x
```






# Gate Level Primitive

 

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

# Gate Level Primitive

 

$$g = x_1x_3 + x_2x_4$$

$$h = (x_1 + \bar{x}_3)(\bar{x}_2 + x_4)$$

$$f = g + h$$

```
module example2 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  and (z1, x1, x3);  
  and (z2, x2, x4);  
  or (g, z1, z2);  
  or (z3, x1, ~x3);  
  or (z4, ~x2, x4);  
  and (h, z3, z4);  
  or (f, g, h);
```

```
endmodule
```

# Summary

- **Structural modeling style** – design described using basic logic gates (and, or, not, xor, buf, bufif, notif, etc.)
- **Represents actual hardware connections** – closer to physical circuits (netlists).
- **Supports strength modeling** – logic strengths (strong, weak, supply) and signal states (0, 1, x, z).
- **Useful for small circuits**, switches, tri-state buffers (bufif, notif).
- **Limitations – Not practical** for large designs (tedious, error-prone).



Thank you !

Happy Learning