

Verilog HDL: Vectors

Pravin Zode

Outline

- Introduction to vectors
- Packed and Unpacked Arrays
- Bitwise and Logical Operator
- Concatenation Operator
- Replication Operator
- Examples

Vectors

- Vectors group multiple related signals under one name
- Declared with dimensions before the name → `wire [7:0] w;`
- Equivalent to several separate single-bit wires
- Part-select allows access to individual bits → `w[3]`
- Used to simplify circuit connections with multi-bit buses
- Example:
 - `wire [99:0] my_vector; // Declare a 100-element vector`
 - `assign out = my_vector[10]; // Part-select one bit out of the vector`

Declaring Vectors


- Vectors must be declared:
 - `type [upper:lower] vector_name;`
- type specifies the datatype of the vector. This is usually wire or reg.
- Input or output ports can also include their type in the declaration (e.g., input wire a;, output reg y;)
- Endianness defines the bit order in a vector
 - **Little-endian:** LSB has the lower index → [3:0]
 - **Big-endian:** LSB has the higher index → [0:3]

Examples

- `wire [7:0] w;` // 8-bit wire
- `reg [4:1] x;` // 4-bit reg
- `output reg [0:0] y;` // 1-bit reg that is also an output port (this is still a vector)
- `input wire [3:-2] z;` // 6-bit wire input (**negative ranges are allowed**)
- `output [3:0] a;` // 4-bit output wire. Type is 'wire' unless specified otherwise.
- `wire [0:7] b;` // 8-bit wire where b[0] is the most-significant bit.

 Exercise-01

- Build a circuit that has one 3-bit input, then outputs the same vector, and also splits it into three separate 1-bit outputs. Connect output o0 to the input vector's position 0, o1 to position 1, etc...




Implicit nets

- Created automatically if a signal is undeclared
- Can arise from an assign statement or undeclared module port
- Always treated as 1-bit wires
- Leads to bugs if a vector was intended
- Prevent implicit nets using: ``default_nettype none`

 Example: Implicit nets

- Without default_nettype none (**bug due to implicit net**)

```
module implicit_example(input a, input b, output y);  
    assign y = a & bb;    // Typo: "bb" instead of "b"  
Endmodule  
// Here, bb is not declared, so Verilog creates an  
implicit 1-bit wire.
```



- With default_nettype none (**error detected**)

```
`default_nettype none  
module implicit_example(input a, input b, output y);  
    assign y = a & bb;    // Compiler ERROR: "bb" undeclared  
endmodule  
`default_nettype wire  
// compiler throws an error instead of silently creating a  
wrong wire.
```


Example: Implicit nets

- Without default_nettype none (**bug due to implicit net**)

```
module implicit_example(input a, input b, output y);  
    assign y = a & bb;    // Typo: "bb" instead of "b"  
Endmodule  
// Here, bb is not declared, so Verilog creates an  
implicit 1-bit wire.
```

- With default_nettype none (**error detected**)

```
`default_nettype none  
module implicit_example(input a, input b, output y);  
    assign y = a & bb;    // Compiler ERROR: "bb" undeclared  
endmodule  
`default_nettype wire  
// compiler throws an error instead of silently creating a  
wrong wire.
```

Example: Implicit nets

- Disabling creation of implicit nets can be done using the ``default_netttype none` directive.

```
wire [2:0] a, c;    // Two vectors
assign a = 3'b101;  // a = 101
assign b = a;       // b = 1  implicitly-created
wire
assign c = b;       // c = 001  <-- bug
my_module i1 (d,e); // d and e are implicitly one-bit
wide if not declared.

                // This could be a bug if the port
was intended to be a vector.
```

Unpacked vs. Packed Arrays

- **Packed arrays:**
 - Declared with indices before the name
 - Bits are stored together as a vector
 - Example: `reg [7:0] data; // 8-bit packed vector`
- **Unpacked arrays:**
 - Declared with indices after the name
 - Represent multiple elements (like memory)
 - Example: `reg [7:0] mem [255:0]; // 256 elements of 8-bit vectors`
 - `reg mem2 [28:0]; // 29 elements of 1-bit regs`
- **Usage:** **Packed** → represent buses / vectors
Unpacked → represent memories / arrays

Exercise


- Build a combinational circuit that splits an input half-word (16 bits, [15:0]) into lower [7:0] and upper [15:8] bytes.

```
`default_nettype none           // Disable implicit nets.  
                                  Reduces some types of bugs.
```

```
module top_module(  
    input wire [15:0] in,  
    output wire [7:0] out_hi,  
    output wire [7:0] out_lo );
```


Write your code here

```
endmodule
```

 

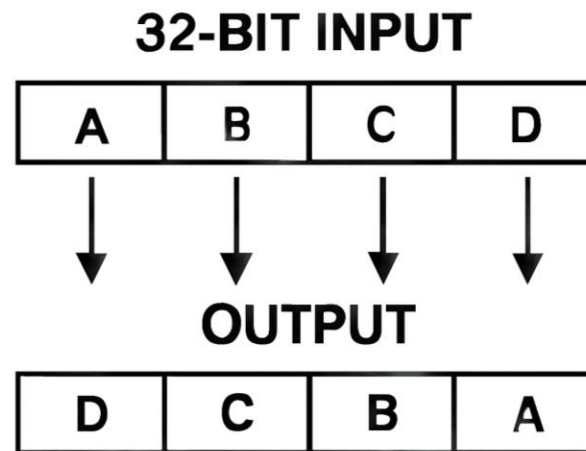
Exercise

- A 32-bit vector can be viewed as containing 4 bytes (bits [31:24], [23:16], etc.). Build a circuit that will reverse the byte ordering of the 4-byte word.
- **AAAAAAAABBBBBBBBCCCCCCCCDDDDDDDD =>
DDDDDDDDCCCCCCCCBBBBBBBBAAAAAAAA**



 
Exercise : Bitwise vs. Logical Operators

- Build a circuit that has two 3-bit inputs that computes the bitwise-OR of the two vectors, the logical-OR of the two vectors, and the inverse (NOT) of both vectors. Place the inverse of b in the upper half of out_not (i.e., bits [5:3]), and the inverse of a in the lower half. out_not



 Exercise : Multiple Input Gates

- Build a combinational circuit with four inputs, in[3:0].
- There are 3 outputs:
 - **out_and**: output of a 4-input AND gate.
 - **out_or**: output of a 4-input OR gate.
 - **out_xor**: output of a 4-input XOR gate.



Part Selection and Concatenation

- **Part Selection** : Used to select portions of a vector.
- **Concatenation Operator { }** : Creates larger vectors by joining smaller ones
- Examples:
 - $\{3'b111, 3'b000\} \rightarrow 6'b111000$
 - $\{1'b1, 1'b0, 3'b101\} \rightarrow 5'b10101$
 - $\{4'ha, 4'd10\} \rightarrow 8'b10101010$
 - Rule: All components must have defined width. $\{1, 2, 3\}$ ❌
Illegal \rightarrow Error: unsized constants not allowed

Example : Concatenation

```
input  [15:0] in;  
output [23:0] out;
```

```
assign {out[7:0], out[15:8]} = in;           // Swap two bytes  
assign out[15:0] = {in[7:0], in[15:8]};     // Same as above  
assign out = {in[7:0], in[15:8]};           // Extended to 24-  
                                              bit, out[23:16] = 0
```


Exercise :

- Inputs: six 5-bit vectors $\rightarrow a, b, c, d, e, f \rightarrow 30$ bits
- Outputs: four 8-bit vectors $\rightarrow w, x, y, z \rightarrow 32$ bits
- Requirement: Concatenate all inputs + two 1 bits

```
assign {w, x, y, z} = {a, b, c, d, e, f, 2'b11};
```

 
Exercise

- Given an 8-bit input vector [7:0], reverse its bit ordering




Replication Operator

 - Used to repeat a vector multiple times
- Shorthand to avoid tedious concatenation
- Requires two braces: `{ num { vector } }`
- `{3{4'b1010}}` // This results in 12 bits:
`1010_1010_1010`



 
Exercise-1: Replication Operator

- Build a circuit that sign-extends an 8-bit number to 32 bits. This requires a concatenation of 24 copies of the sign bit (i.e., replicate bit[7] 24 times) followed by the 8-bit number itself.



 Exercise-2 : Replication Operator

- Given five 1-bit signals (a, b, c, d, and e), compute all 25 pairwise one-bit comparisons in the 25-bit output vector. The output should be 1 if the two bits being compared are equal



Conclusion



- **Vectors:** Represent multi-bit signals efficiently
- **Packed & Unpacked Arrays:** Organize data in structured formats
- **Concatenation Operator {}:** Joins smaller vectors into larger ones
- **Replication Operator {num{vector}}:** Repeats vectors compactly
- **Bitwise Operators (& | ^ ~):** Operate on signals bit by bit
- **Logical Operators (&& || !):** Evaluate overall true/false conditions.

→ data [15:0] ←

a[1] / b(7.0)

ZAP!

vector

  

Thank you !

Happy Learning