


Verilog HDL: Examples : Sequential Circuits

Pravin Zode

Outline

- D-Latch and D-FF
- Reset(Synchronous & Asynchronous)
- SR Latch
- JK Flip-Flop
- Shift Register
- Counters

Types of Triggering

 

D-Latch & D-FF

```
1  module latch (D, clk, Q);
2  input D, clk;
3  output reg Q;
4  always @(D, clk)
5  if (clk)
6  |   Q = D;
7  endmodule
```

D-Latch

```
1  module flipflop (D, Clock, Q);
2  input D, Clock;
3  output reg Q;
4  always @(posedge Clock)
5  |   Q <= D;
6  endmodule
```

D-FlipFlop

D-Latch & D-FF

```
1  module latch (D, clk, Q);
2  input D, clk;
3  output reg Q;
4  always @(D, clk)
5  if (clk)
6  |   Q = D;
7  endmodule
```

D-Latch

```
1  module flipflop (D, Clock, Q);
2  input D, Clock;
3  output reg Q;
4  always @(posedge Clock)
5  |   Q <= D;
6  endmodule
```

D-FlipFlop

Reset (Synchronous & Asynchronous)

Synchronous Reset (waits for clock edge)

```
always @(posedge clk) begin
    if (reset) q <= 0;
    else      q <= q + 1;
end
```

Resets q to 0 only on
the rising edge of clk

Asynchronous Reset (immediate reset)

```
always @(posedge clk or posedge reset) begin
    if (reset)
        q <= 0;
    else
        q <= q + 1;
end
```

Resets q to 0 as soon as reset
goes high, even if clock
hasn't ticked

Flip-Flop Synchronous & Asynchronous Reset


```
1  module flipflop_ar (D, Clock, Resetn, Q);
2  input D, Clock, Resetn;
3  output reg Q;
4  always @(posedge Clock, negedge Resetn)
5  if (Resetn == 0)
6  |   Q <= 0;
7  else
8  |   Q <= D;
9  endmodule
```

D flip-flop with
synchronous reset

D flip-flop with
asynchronous reset

```
1  module flipflop_sr (D, Clock, Resetn, Q);
2  input D, Clock, Resetn;
3  output reg Q;
4  always @(posedge Clock)
5  ✓ if (Resetn == 0)
6  |   Q <= 0;
7  ✓ else
8  |   Q <= D;
9  endmodule
```


SR Latch

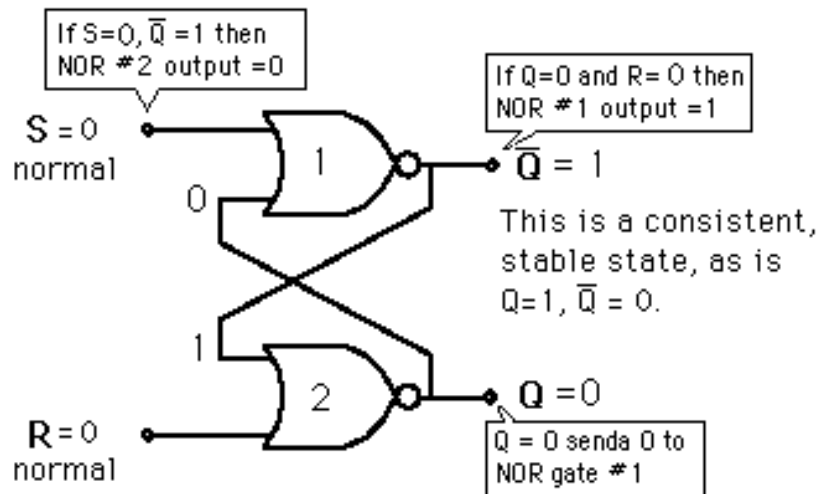

Truth Table

Set	Reset	Output
0	0	No change*
1	0	$Q=1$
0	1	$Q=0$
1	1	Invalid state

*can be used for data storage

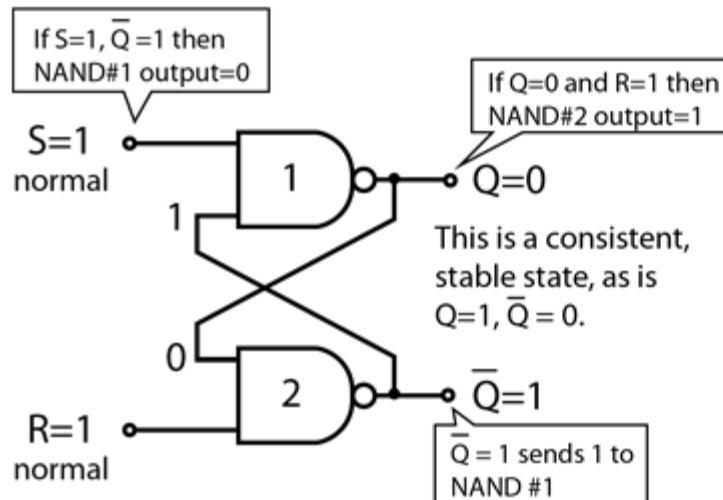

Truth Table

Set	Reset	Output
1	1	No change*
0	1	$Q=1$
1	0	$Q=0$
0	0	Invalid state

* can be used for data storage

SR Latch

Dataflow Model

```
// SR Latch using NOR gates
module sr_latch (
    input S, // Set input
    input R, // Reset input
    output Q, // Normal output
    output Qbar // Complement
);

    // Cross-coupled NOR gates
    assign Q      = ~(R | Qbar);
    assign Qbar   = ~(S | Q);

endmodule
```

Gate Level Model

```
// SR latch - gate-level
modeling using NOR primitives
module sr_latch_gatelevel (
    input  S,    // Set
    input  R,    // Reset
    output Q,    // Normal output
    output Qbar // Complement
);

    nor u1(Q,R, Qbar);
    nor u2(Qbar, S, Q);

endmodule
```

SR Flip-Flop (version-1)


```
// Clocked SR FF (Behavioral using if-else with explicit condn)
module sr_ff_ifelse (
    input  clk,      // Clock input
    input  S,        // Set input
    input  R,        // Reset input
    output reg Q,    // Normal output
    output reg Qbar  // Complement output
);
    always @(posedge clk) begin
        if (S==1 && R==0)
            Q <= 1;           // Set
        else if (S==0 && R==1)
            Q <= 0;           // Reset
        else if (S==0 && R==0)
            Q <= Q;           // Hold (no change)
        else if (S==1 && R==1)
            Q <= 1'bx;        // Invalid case
    end
    assign Qbar = ~Q;
endmodule
```

SR Flip-Flop (version-2)

```
// Clocked SR Flip-Flop (Behavioral using if-else)
module sr_ff_ifelse (
    input  clk,      // Clock input
    input  S,        // Set input
    input  R,        // Reset input
    output reg Q,    // Normal output
    output reg Qbar  // Complement output
);
    always @(posedge clk) begin
        if (S && ~R)
            Q <= 1;           // Set
        else if (~S && R)
            Q <= 0;           // Reset
        else if (~S && ~R)
            Q <= Q;           // Hold (no change)
        else
            Q <= 1'bx;        // Invalid case (S=R=1)
    end
    assign Qbar = ~Q;
endmodule
```

JK Flip-Flop (version-1)

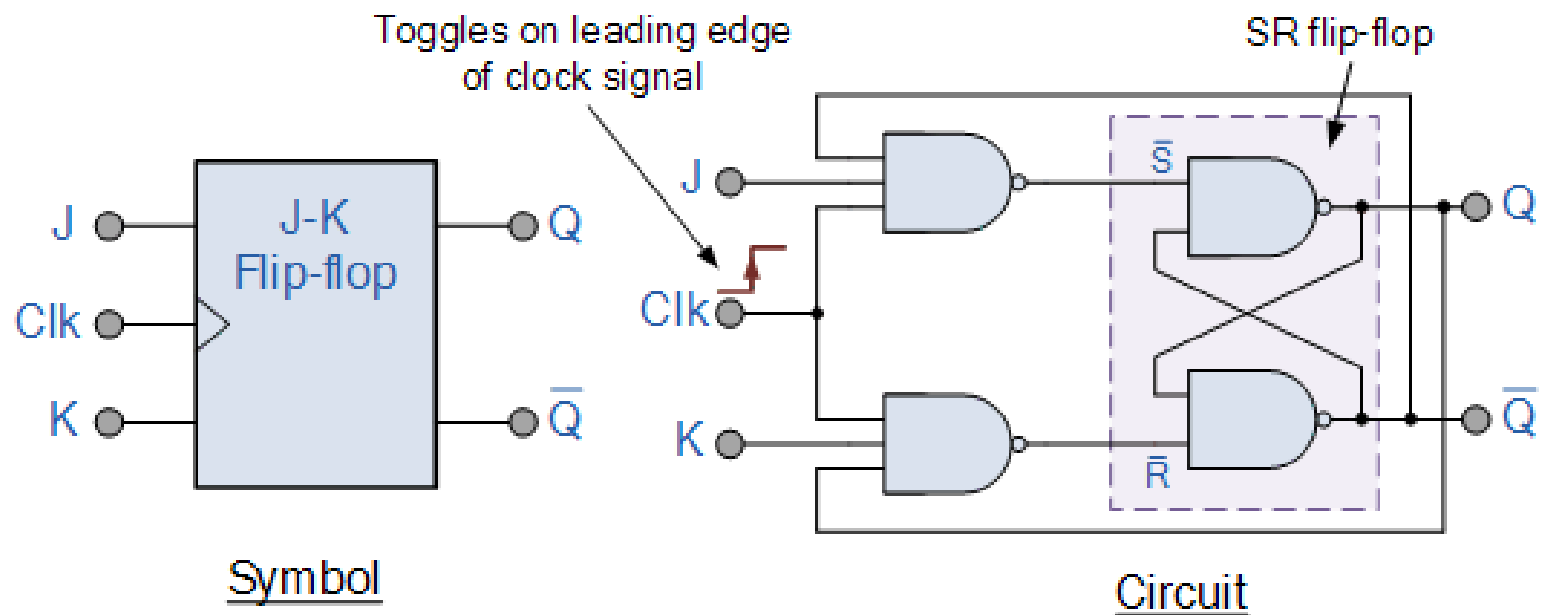- It is modified version of SR FF invented by Jack Kilby from Texas Instruments



JK Flip-Flop Truth Table

	Clock	Input		Output		Description
	Clk	J	K	Q	Q	
same as for the SR Latch	X	0	0	1	0	Memory no change
	X	0	0	0	1	
	$\overline{\downarrow}$	0	1	1	0	Reset Q » 0
	X	0	1	0	1	
	$\overline{\downarrow}$	1	0	0	1	Set Q » 1
	X	1	0	1	0	
toggle action	$\overline{\downarrow}$	1	1	0	1	Toggle
	$\overline{\downarrow}$	1	1	1	0	


JK Flip-Flop Verilog Code (Version-1)

```
// JK Flip-Flop (Behavioral, using if-else)
module jk_ff (
    input  clk,      // Clock input
    input  J,        // J input
    input  K,        // K input
    output reg Q,    // Normal output
    output  Qbar     // Complement output
);
    always @(posedge clk) begin
        if (J==0 && K==0)
            Q <= Q;           // Hold (no change)
        else if (J==0 && K==1)
            Q <= 0;           // Reset
        else if (J==1 && K==0)
            Q <= 1;           // Set
        else if (J==1 && K==1)
            Q <= ~Q;          // Toggle
    end
    assign Qbar = ~Q;
endmodule
```

JK Flip-Flop Verilog Code (Version-2)

```
// JK Flip-Flop (Behavioral, using case statement)
module jk_ff_case (
    input  clk,      // Clock input
    input  J,        // J input
    input  K,        // K input
    output reg Q,    // Normal output
    output  Qbar    // Complement output
);
    always @(posedge clk) begin
        case ({J,K})
            2'b00: Q <= Q;      // Hold (no change)
            2'b01: Q <= 1'b0;   // Reset
            2'b10: Q <= 1'b1;   // Set
            2'b11: Q <= ~Q;     // Toggle
        endcase
    end
    assign Qbar = ~Q;
endmodule
```

Shift Register

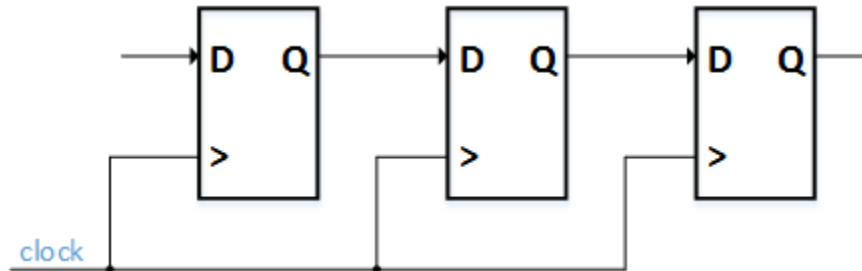

```
1  module shift3 (w, Clock, Q);
2  input w, Clock;
3  output reg [1:3] Q;
4  always @(posedge Clock)
5  begin
6      Q[3] <= w;
7      Q[2] <= Q[3];
8      Q[1] <= Q[2];
9  end
10 endmodule
```

Three-bit shift register

```
1  module shift3 (w, Clock, Q);
2  input w, Clock;
3  output reg [1:3] Q;
4  always @(posedge Clock)
5  begin
6      Q[3] = w;
7      Q[2] = Q[3];
8      Q[1] = Q[2];
9  end
10 endmodule
```

**Wrong code for a
three-bit shift register**



Shift Register

```
1  module shiftreg_4bit (clock, clear, A, E);
2  input clock, clear, A;
3  output reg E;
4  reg B, C, D;
5  always @(posedge clock or negedge clear)
6  begin
7  if (!clear)
8  begin
9  |   B<=0; C<=0; D<=0; E<=0;
10 end
11 else
12 begin
13 |   E <= D;
14 |   D <= C;
15 |   C <= B;
16 |   B <= A;
17 end
18 end
19 endmodule
```

```
1  module shiftreg_4bit_tb;
2  reg clk, clr, in; wire out; integer i;
3  shiftreg_4bit SR (clk, clr, in, out);
4  initial
5  begin clk = 1'b0; #2 clr = 0; #5 clr = 1;
6  end
7  always #5 clk = ~clk;
8  initial begin #2;
9  repeat (2)
10 begin #10 in=0; #10 in=0; #10 in=1; #10 in=1;
11 end
12 end
13 initial
14 begin
15 $dumpfile ("shifter.vcd");
16 $dumpvars (0, shift_test);
17 #200 $finish;
18 end
19 endmodule
```


Shift Register (Loadable)

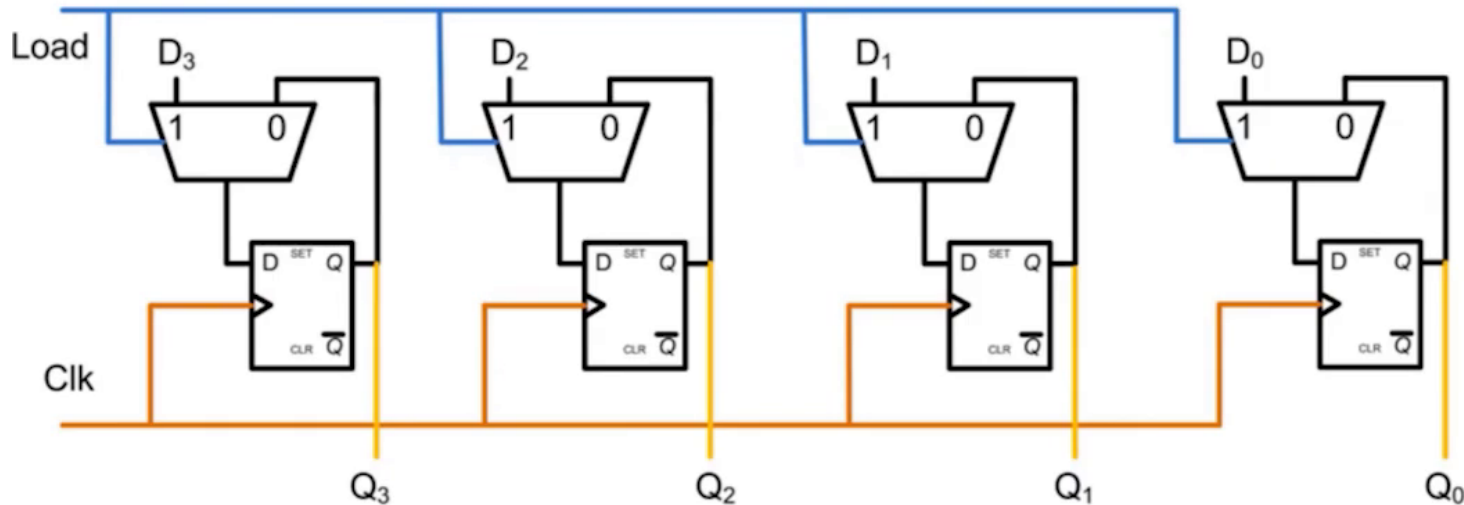 - Load signal is used to decide the operation
- If load =0, it holds
- If load =1, it load new value



Shift Register (Clear & Loadable)

 - load and clear decides the operation
- if clear is 1, load is not considered, and output is 0
- if load = 0, it holds
- if load = 1, it loads new value



Extend this to 4-bit shift register

- **Purpose of Counters**

- Used to count various operations and events
- Store and display the number of occurrences and repetitions



- **Types of Counters**

- Synchronous Counters – all flip-flops triggered by the same clock
- Asynchronous Counters – flip-flops triggered in sequence

- **Implementation**

- Mostly designed using JK Flip-Flops (JK FFs)

Asynchronous Counter

 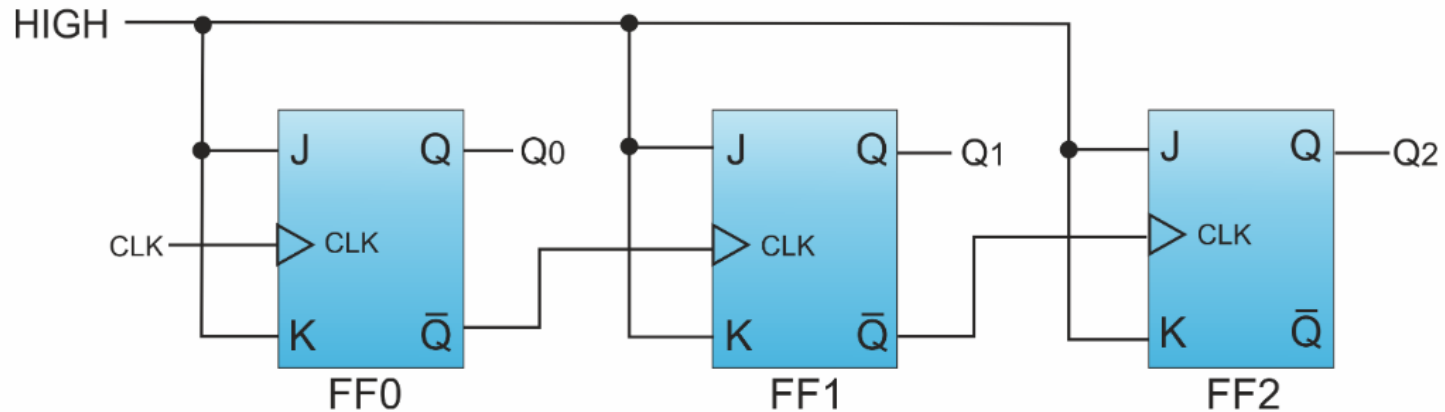

Asynchronous Up-Counter

```
1  module async_counter(  
2      input clk,  
3      output reg [3:0] count );  
4  
5      initial count = 0;  
6  
7      always @(posedge clk) begin  
8          count[0] <= ~count[0];  
9      end  
10  
11     always @(posedge count[0]) begin  
12         count[1] <= ~count[1];  
13     end  
14  
15     always @(posedge count[1]) begin  
16         count[2] <= ~count[2];  
17     end  
18  
19     always @(posedge count[2]) begin  
20         count[3] <= ~count[3];  
21     end  
22  
23 endmodule
```


Pattern Counter-Ring Counter

- A circular shift register where the output of the last flip-flop is fed back to the first.
 - Requires n flip-flops for n states.
 - Example: 4-bit Ring Counter \rightarrow 4 states
- $1000 \rightarrow 0100 \rightarrow 0010 \rightarrow 0001 \rightarrow 1000 \dots$
- Applications:
 - Sequence generation
 - Timing signals
 - Control logic

Pattern Counter-Ring Counter

- The ring counter is application of shift register, in which the output of last flip flop is connected to input of first flip flop
- In ring counter if the output of any flip flop is 1, then the output of remaining flip flops is 0.


RING COUNTER

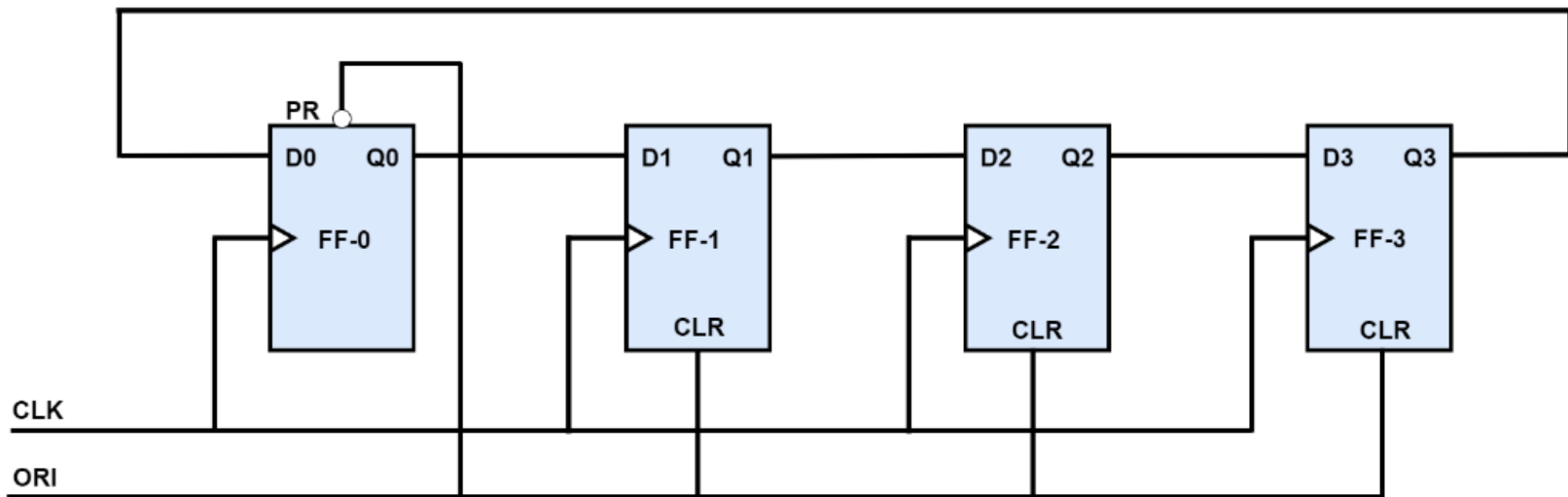

Pattern Counter-Johnson Counter

A Johnson counter is a type of shift register counter where the inverted output of the last flip-flop is fed back to the input of the first flip-flop (Twisted Ring Counter)

JOHNSON'S COUNTER

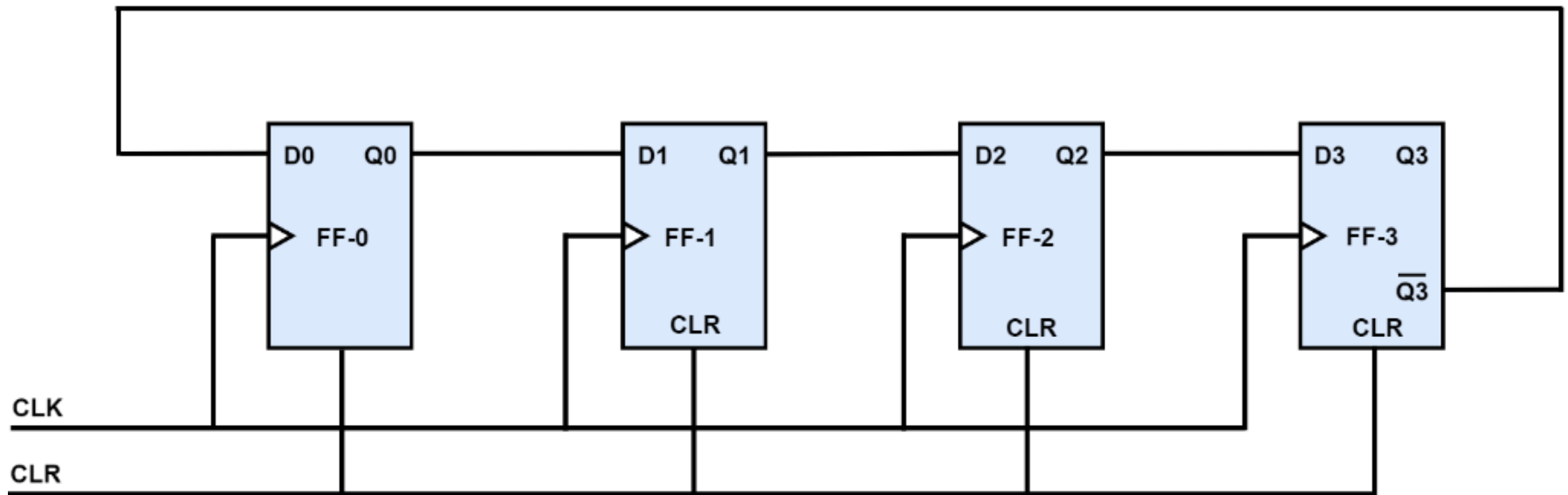

Pattern Counter-Johnson Counter

Clock no.	D3	D2	D1	D0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0
9	1	0	0	0

```
1  module Counter_4_Johnson(clk,reset,count);
2  input clk,reset;
3  output reg[3:0]count;
4  reg [3:0]temp;
5  always @(posedge clk or reset)
6  begin
7  if (reset==1)
8  |   temp =4'b0000;
9  else
10 begin
11 |   temp = {~temp[0],temp[3:1]};
12 end
13 assign count =temp;
14 end
15 endmodule
```

Counter

```
1  module counter (clear, clock, count);
2  parameter N = 7;
3  input clear, clock;
4  output reg [0:N] count;
5  always @(negedge clock)
6  if (clear)
7  |   count <= 0;
8  else
9  |   count <= count + 1;
10 endmodule

1  module test_counter;
2  reg clk, clr;
3  wire [7:0] out;
4  counter CNT (clr, clk, out);
5  initial clk = 1'b0;
6  always #5 clk = ~clk;
7  initial
8  begin
9  clr = 1'b1;
10 #15 clr = 1'b0;
11 #200 clr = 1'b1;
12 #10 $finish;
13 end
14 initial
15 begin
16 $dumpfile ("counter.vcd");
17 $dumpvars (0, test_counter);
18 $monitor ($time, " Count: %d", out);
19 end
20 endmodule
```

Clock Divider

LED Blinking Example

```
1  module ledblink(clk,led);
2  input clk; output led; reg led;
3
4  reg[23:0] cnt;
5
6  always @(posedge clk)
7  begin
8      cnt<= cnt + 1'b1;
9      led<=cnt[23];
10 end
11 endmodule
```



Thank you !

Happy Learning