

Assignment-02 (Conditional Operator)

Write Verilog code using conditional operator

1. 4:1 multiplexer
2. 4:2 Binary Encoder
3. 1:4 Demultiplexer
4. 4-bit Magnitude comparator
5. 4-Bit Priority Encoder