

Assignment -06 : Procedural Assignments

Using Case, Casex and Casez

- 8:1 Multiplexer
- 1:8 Demultiplexer
- JK FF using case statement
Write code for HEX to seven segment decoder using **case statement**
- Write code for ALU using **case statement**, refer following table

Operation	Inputs			Outputs			
	s_2	s_1	s_0	F			
Clear	0	0	0	0	0	0	0
B-A	0	0	1	$B - A$			
A-B	0	1	0	$A - B$			
ADD	0	1	1	$A + B$			
XOR	1	0	0	$A \text{ XOR } B$			
OR	1	0	1	$A \text{ OR } B$			
AND	1	1	0	$A \text{ AND } B$			
Preset	1	1	1	1	1	1	1

- **Simple Pattern Detector (casex) :** Design a module that uses a casex statement to detect a specific pattern (e.g., if the MSB of a 3-bit input is 1) and assert an output signal.
- **BCD to 7-Segment Display Decoder (casez) :** Build a decoder that converts a 4-bit BCD input into a 7-segment display output, using casez to manage any high-impedance or don't care conditions in the input.
- **Digital Lock System (casez) :** Design a digital lock module that validates an input code using casez to allow for partial matching (don't cares) in the sequence, outputting an unlock signal when the correct pattern is detected.
- **Priority Encoder (casez) :** Design a priority encoder that outputs the highest priority active input from an 8-bit signal, using casez to simplify handling of don't care conditions.