


Verilog HDL: Finite State Machines

Pravin Zode

Outline

- Mealy and Moore Machines
- Implementation Steps
- Exercises

Synchronous Sequential Machines

 


Introduction

- FSM is a sequential circuit that transitions through a finite number of states.
- Behavior is defined by current state and input.
- FSM = Combinational Logic + Memory (Flip-Flops)
- **Applications:** Protocol design, traffic lights, vending machines, control units


Types of FSM

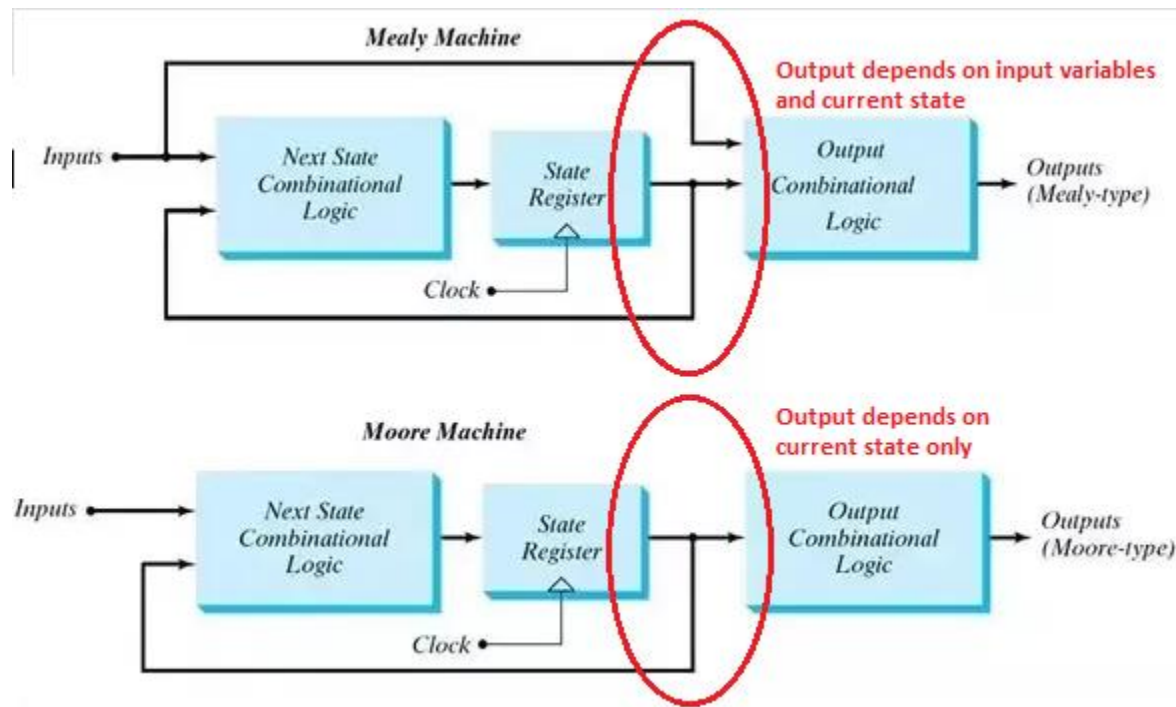- Moore Machine: Output depends only on the current state
- Mealy Machine: Output depends on current state and input



Output from State Machine

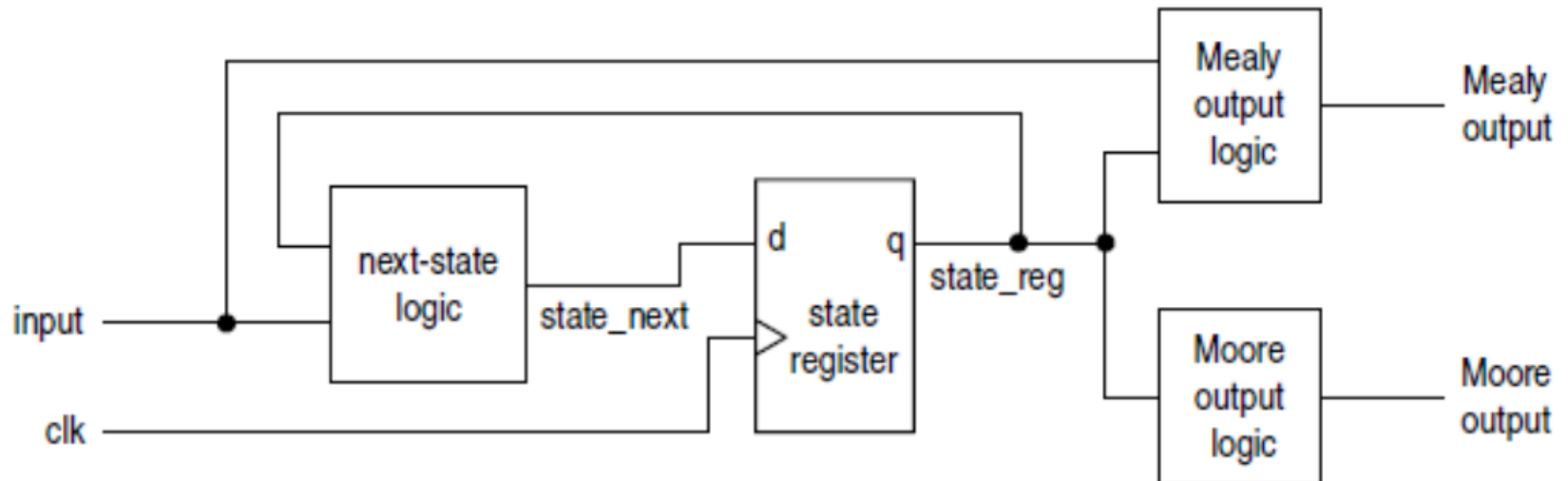- Moore Machine: Output depends only on the current state
- Mealy Machine: Output depends on current state and input





FSM Design Steps


- Define the states
- Draw the state transition diagram
- Create the state transition table
- Encode states (binary/gray/one-hot)
- Write Verilog code
 - State register
 - Next-state logic
 - Output logic
- Test using simulation.

Moor Machine (101 Detector)

- Define

  

Mealy Machine (101 Detector)

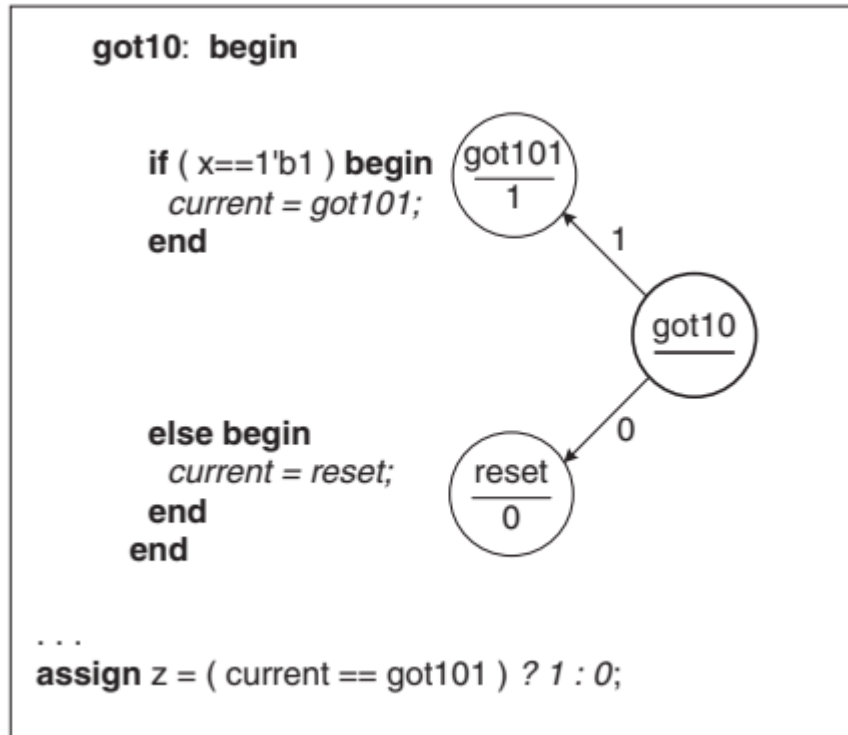

```


`timescale 1ns/100ps

module moore_detector (input x, rst, clk, output z);
    localparam [1:0]
        reset=0, got1=1, got10=2, got101=3;
    reg [1:0] current;
    always @( posedge clk ) begin
        if( rst ) current <= reset;
        else case ( current )
            reset: begin
                if( x==1'b1 ) current <= got1;
                else current <= reset;
            end
            got1: begin
                if( x==1'b0 ) current <= got10;
                else current <= got1;
            end
            got10: begin
                if( x==1'b1 ) current <= got101;
                else current <= reset;
            end
            got101: begin
                if( x==1'b1 ) current <= got1;
                else current <= got10;
            end
            default: begin
                current <= reset;
            end
        endcase
    end

    assign z = (current==got101) ? 1 : 0;
endmodule

```

 Moore Machine (101/110 Detector) Overlapping



Moore Machine (101/110 Detector) Overlapping



```
`timescale 1ns/100ps
```

```
`define reset      3'b000
`define got1       3'b001
`define got10      3'b010
`define got11      3'b011
`define got101     3'b100
`define got110     3'b101
```


```
module moore_detector3 (input x, rst, clk, output z);
    reg [2:0] current;
    always @( posedge clk or posedge rst ) begin
        if( rst ) current = `reset;
        else
            case ( current )
                `reset:
                    if( x==1'b1 ) current <= `got1;
                    else current <= `reset;
                `got1:
                    if( x==1'b0 ) current <= `got10;
                    else current <= `got11;
                `got10:
                    if( x==1'b1 ) current <= `got101;
                    else current <= `reset;
                `got11:
                    if( x==1'b1 ) current <= `got11;
                    else current <= `got110;
                `got101:
                    if( x==1'b1 ) current <= `got11;
                    else current <= `got10;
                `got110:
                    if( x==1'b1 ) current <= `got101;
                    else current <= `reset;
                default:
                    current <= `got101;
            endcase
        end

        assign z = (current == `got101 || current == `got110);
    endmodule
```

Mealy Machine (101) Overlapping

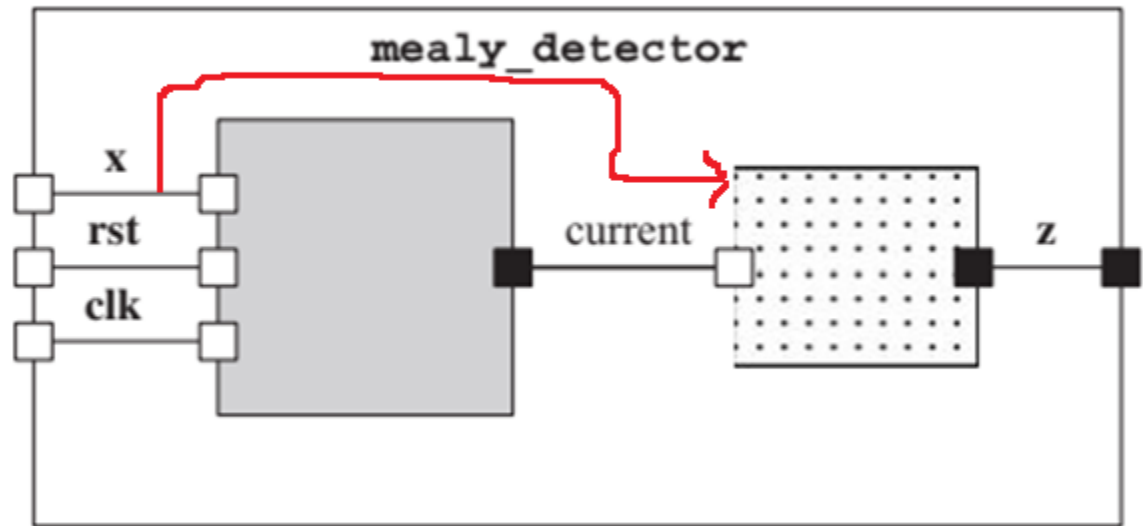 

Mealy Machine (101) Overlapping

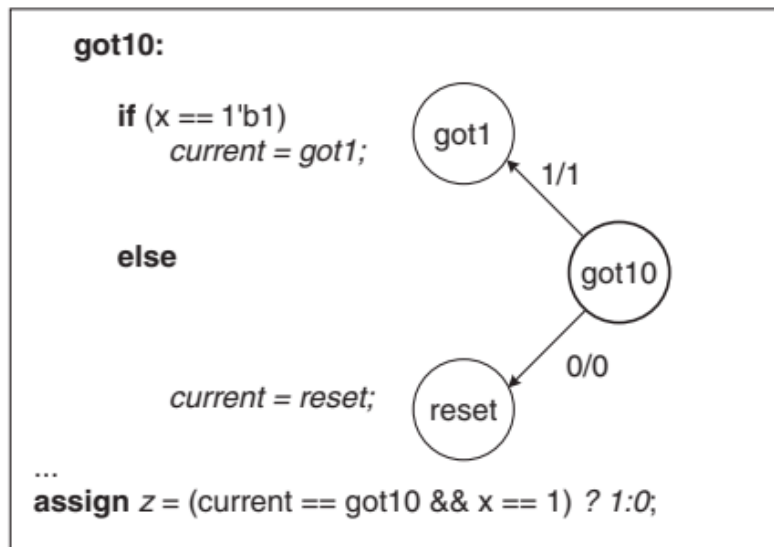

```
`timescale 1ns/100ps

module mealy_detector2 (input x, rst, clk, output z);

    localparam [1:0]
        reset = 0, // 0 = 0 0
        got1 = 1, // 1 = 0 1
        got10 = 2; // 2 = 1 0

    reg [1:0] current;


    always @( posedge clk ) begin
        if (rst) current <= reset;
        else case ( current )
            reset:
                if( x==1'b1 ) current <= got1;
                else current <= reset;
            got1:
                if( x==1'b0 ) current <= got10;
                else current <= got1;
            got10:
                if( x==1'b1 ) current <= got1;
                else current <= reset;
            default:
                current <= reset;
        endcase
    end

    assign z = ( current==got10 && x==1'b1 ) ? 1'b1 : 1'b0;


endmodule
```

Sequence Detector (1010)

Overlapping Not Allowed

 

 Sequence Detector (1010) Overlapping Allowed



FSM Coding Style


State Register (with synchronous reset):

```
always @(posedge clk) begin
    if (reset)
        state <= IDLE;
    else
        state <= next_state;
end
```

Next-State Logic


```
✓ always @(*) begin
✓     case(state)
        IDLE: next_state = (in) ? S1 : IDLE;
        S1:   next_state = (in) ? S2 : IDLE;
        ...
    endcase
end
```


Moore Machine

 


Next-State Logic

Sequential Adder

 

 
$$\begin{array}{r}
 t_5 \quad t_4 \quad t_3 \quad t_2 \quad t_1 \\
 0 \quad 1 \quad 1 \quad 0 \quad 0 = X_1 \\
 + \quad 0 \quad 1 \quad 1 \quad 1 \quad 0 = X_2 \\
 \hline
 1 \quad 1 \quad 0 \quad 1 \quad 0 = Z
 \end{array}$$




PS	NS, z			
	$x_1x_2 = 00$	01	11	10
A	A, 0	A, 1	B, 0	A, 1
B	A, 1	B, 0	B, 1	B, 0

Sequential Adder

 

		NS, z			
PS	$x_1x_2 = 00$	01	11	10	
A	$A, 0$	$A, 1$	$B, 0$	$A, 1$	
B	$A, 1$	$B, 0$	$B, 1$	$B, 0$	

 


		Next state Y				Output z			
		<hr/>				<hr/>			
	x_1x_2					x_1x_2			
y	00	01	11	10	00	01	11	10	
<hr/>									
0	0	0	1	0	0	1	0	1	
1	0	1	1	1	1	0	1	0	
<hr/>									

Sequence Detector (0101)

Input 010101

Output 000101

 

<i>PS</i>	<i>NS, z</i>	
	<i>x = 0</i>	<i>x = 1</i>
<i>A</i>	<i>B, 0</i>	<i>A, 0</i>
<i>B</i>	<i>B, 0</i>	<i>C, 0</i>
<i>C</i>	<i>D, 0</i>	<i>A, 0</i>
<i>D</i>	<i>B, 0</i>	<i>C, 1</i>

	<i>y₁y₂</i>	<i>Y₁Y₂</i>		<i>z</i>	
		<i>x = 0</i>	<i>x = 1</i>	<i>x = 0</i>	<i>x = 1</i>
<i>A</i>	00	01	00	0	0
<i>B</i>	01	01	11	0	0
<i>C</i>	11	10	00	0	0
<i>D</i>	10	01	11	0	1

Sequence Detector (0101)

		Y_1Y_2		z	
		$x = 0$	$x = 1$	$x = 0$	$x = 1$
A	00	01	00	0	0
B	01	01	11	0	0
C	11	10	00	0	0
D	10	01	11	0	1

$$z = xy_1y'_2,$$

$$Y_1 = x'y_1y_2 + xy'_1y_2 + xy_1y'_2,$$

$$Y_2 = y_1y'_2 + x'y'_1 + y'_1y_2.$$

$y_1y_2 \backslash x$	0	1
00		
01		
11		
10		1

(a) z map.


$y_1y_2 \backslash x$	0	1
00		
01		1
11	1	
10		1

(b) Y_1 map.

$y_1y_2 \backslash x$	0	1
00	1	
01	1	1
11		
10	1	1

(c) Y_2 map.

Sequence Detector (0101)

 

Applications of FSM

- **CPU / Processor Control Unit** – Sequence instructions and generate control signals
- **Sequence Detectors** – Detect specific patterns in serial data (e.g., 101)Communication Protocols – UART, SPI, I2C, Ethernet controllers
- **Counters and Timers** – Up/Down counters, decade counters, programmable timers
- **Traffic Light & Elevator Controllers** – Manage states based on timers or inputs
- **Memory & Storage Controllers** – Manage read/write operations in RAM/FIFO/Cache
- **Vending Machines / Payment Systems** – Track coins, dispense products/change
- **Motor Controllers** – Stepper and servo motor sequencing Test & Diagnostic Systems – Built-in self-test (BIST) for ICs



Thank you !

Happy Learning